



Temperature Control System

Schematic

Create a circuit capable of maintaining four selectable temperature levels (50°C, 75°C, 100°C, 125°C) with an accuracy of $\pm 10^\circ\text{C}$, and include an LED to indicate the heating process.

The circuit should be based on discrete components (not MCU).

Layout

Make the PCB layout of the circuitry